

Exercise 3: SC Circuit


Purpose of the lecture is to get familiar with:

- SC circuits,
- Analysis of SC amplifier
- Analysis and comparison between SC and CT integrators

Exercise 1: Low pass filter and its SC circuit analysis.

Design a low pass passive first order filter with $f_c=1\text{kHz}$ and write a transfer function $H(s)$. Same structure must be realized in discrete z-domain (resistor must be replaced with SC circuit) where transfer function $H(z)$ must be plotted and compared with continuous time $H(s)$ transfer function. Draw the SC schematic. Use `freqs()` and `freqz()` functions.

Draw low pass filter and its corresponding SC schematic

 

Exercise 2: Analysis of inverting and non-inverting SC amplifier

Determine transfer function of the circuits in the Figure 1 and 2. Capacitors must be calculated from the switching frequency $F_s=1$ MHz and its value should not exceed 1 pF. The gain at low frequencies is 40 dB. The characteristics of the opamp and the switches are ideal.

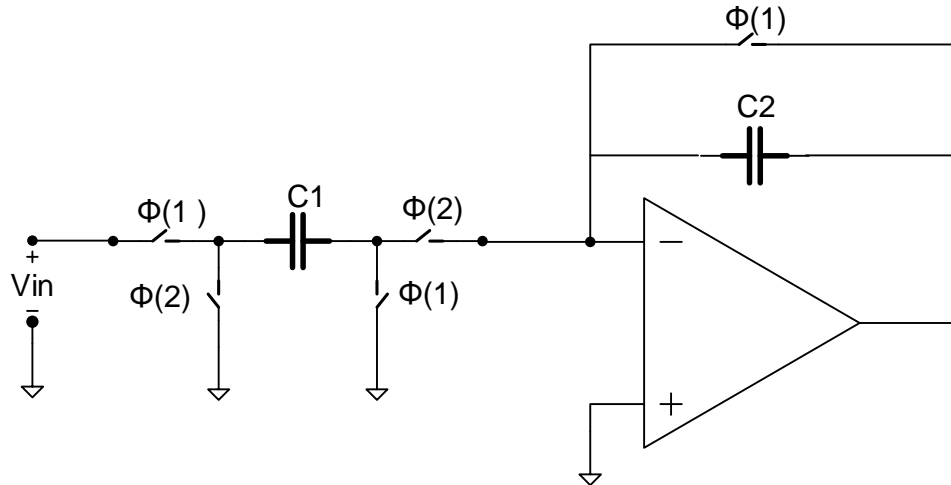


Figure 1: Non-inverting SC amplifier.

$$H(z) =$$

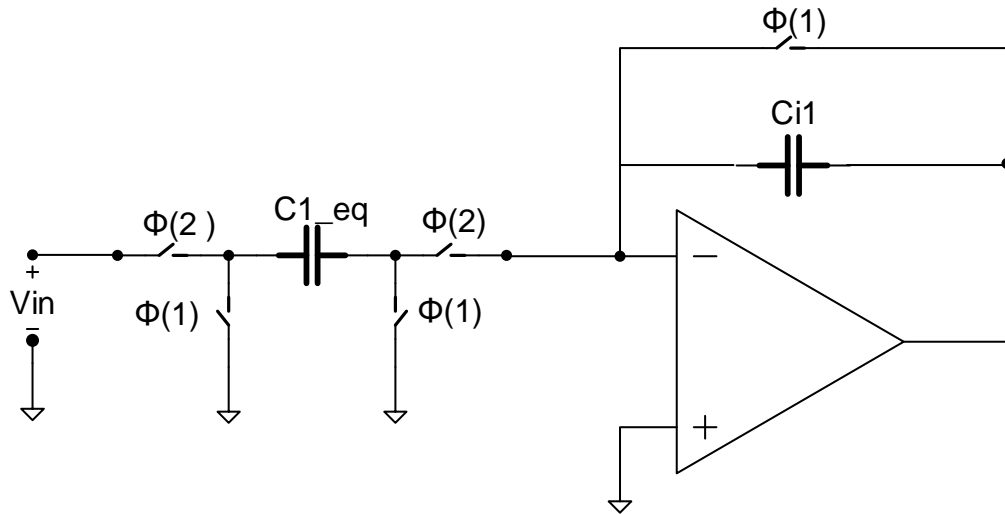


Figure 2: Inverting SC amplifier.

$$H(z) =$$

Exercise 3: Comparison of CT and SC integrators

Calculate transfer function of the integrator in Figure 3. Determine the value of R_1 , R_f and C_f in a way, to achieve low frequency gain of $A_{DC}=10$ with corner frequency $f_c=1$ kHz. Realize SC integrator and replace R_1 and R_f with circuit shown in the Figure 4. For proper inverting operation, it is essential to pay attention to the phases on each switch driven with 1 MHz. Prepare .m file to analyse and compare CT and SC transfer functions. Use `freqs()` and `freqz()` functions.

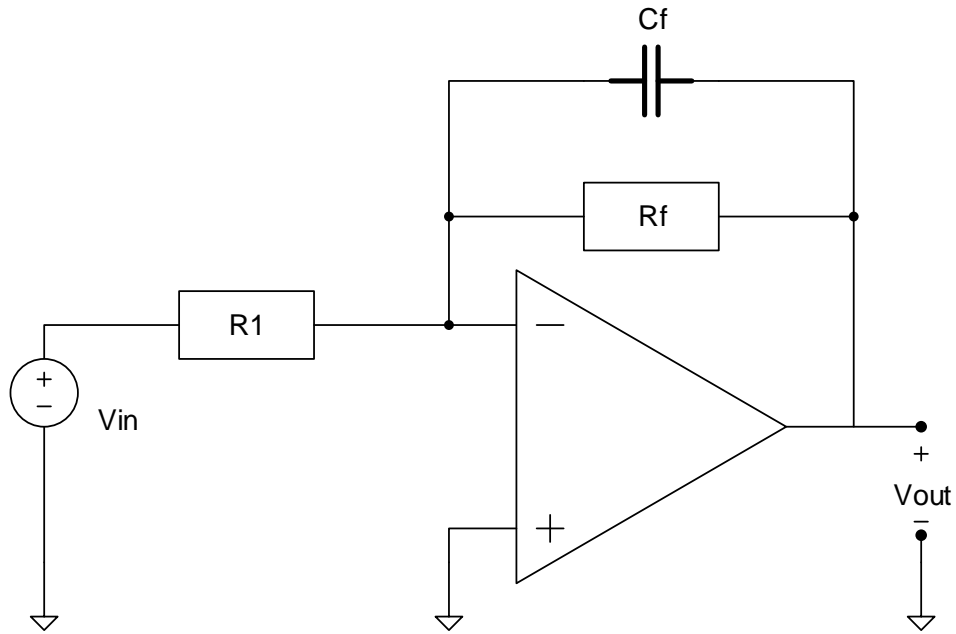


Figure 3: CT integrator.

a) Transfer function of CT integrator (Figure 3)

$$H(s) = \frac{V_{out}}{V_{in}} =$$

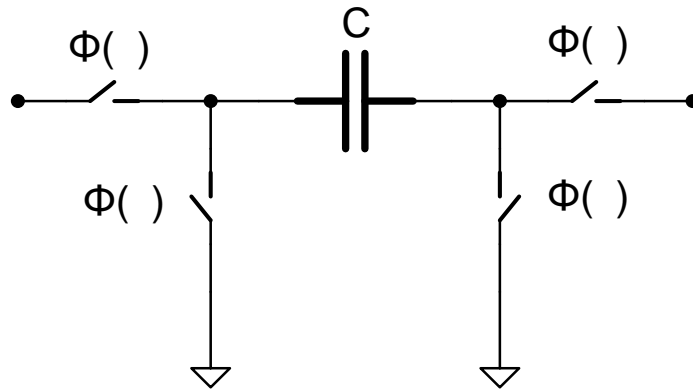


Figure 4: SC realization of resistor.

b) Transfer function of SC integrator (Figure 3)

$$H(z) = \frac{V_{out}}{V_{in}} =$$